

Nome: Gabriel Tetsuo Haga °USP: 11260680

Ex.1 a) · Calor acumulado:  $q = C \frac{d\theta}{dt}$


· Calor recebido:  $q = \frac{\theta_1 - \theta}{m}$

· Pelo balanço de energia:  $q_2 = q_r \Rightarrow C_m \cdot \dot{\theta} = \frac{\theta_b - \theta}{R_m} \Rightarrow$

$$\Rightarrow C_m \cdot R_m \cdot \dot{\theta} + \theta = \theta_b = \boxed{C_m \cdot \dot{\theta} + \theta = \theta_b}$$

$C_m \cdot R_m \rightarrow$  Constante de tempo

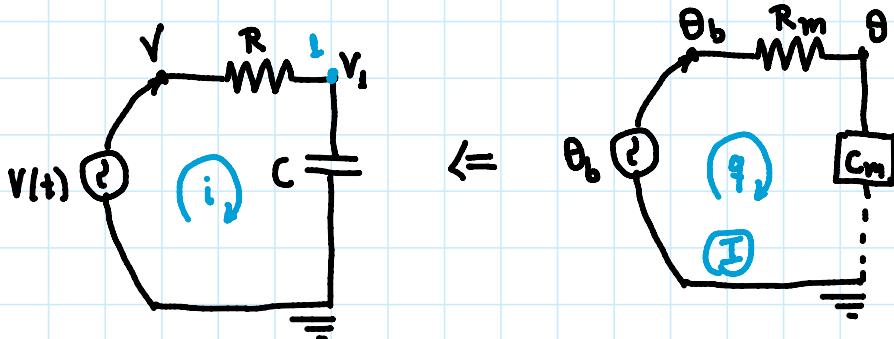b) · Analogia  $\theta \rightarrow V$ ;  $q \rightarrow$



· Método prático: Né 1:

$$V_i \left( CD + \frac{1}{R} \right) - V \cdot \frac{1}{R} = 0$$

· Pela analogia:  $\theta \cdot \left( C_m D + \frac{1}{R_m} \right) - \theta_b \cdot \frac{1}{R_m} = 0 \Rightarrow$

$$\Rightarrow C_m \cdot \dot{\theta} + \frac{\theta}{R_m} = \frac{\theta_b}{R_m} \Rightarrow C_m \cdot R_m \cdot \dot{\theta} + \theta = \theta_b \Rightarrow$$

$$\Rightarrow \boxed{C_m \cdot \dot{\theta} + \theta = \theta_b}$$

Ex.2 a) · Balanço de energia:

→ Mercúrio:

$$C_m \frac{d\theta}{dt} = \theta_V - \Rightarrow \boxed{C_m \frac{d\theta}{dt} + \frac{\theta}{R_m} = \theta_V}$$

→ Mercúrio:

$$C_m \frac{d\theta}{dt} = \theta_v - \frac{\theta}{R_m} \Rightarrow C_m \frac{d\theta}{dt} + \frac{\theta}{R_m} = \theta_v$$


Acumulado    Taxa recebida

→ Vidro:

$$C_v \frac{d\theta_v}{dt} = \frac{\theta_b - \theta_v}{R_v} \Rightarrow C_v \frac{d\theta_v}{dt} + \left( \frac{1}{R_v} + \frac{1}{R_m} \right) \theta_v = \frac{\theta_b}{R_v} + \frac{\theta}{R_m}$$

Acumulado    Taxa perdida para o mercúrio

b) Circuito análogo:

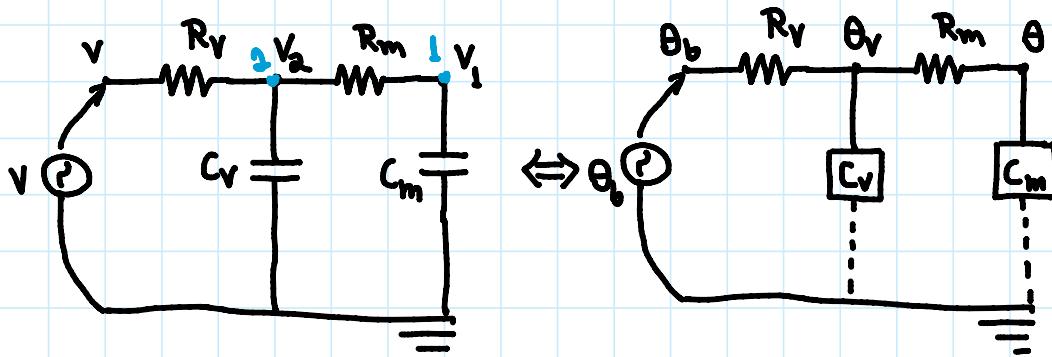

• Pelo método prático:

→ Nô 1:

$$V_1 \left( C_m D + \frac{1}{R_m} \right) - V_2 \cdot \frac{1}{R_m} = 0 \Rightarrow \theta \left( C_m D + \frac{1}{R_m} \right) - \theta_v \cdot \frac{1}{R_m} = 0 \Rightarrow$$


$$\Rightarrow C_m \dot{\theta} + \frac{\theta}{R_m} = \frac{\theta_v}{R_m}$$

→ Nô 2:

$$V_2 \left( C_v D + \frac{1}{R_v} + \frac{1}{R_m} \right) - V_1 \cdot \frac{1}{R_m} - V \cdot \frac{1}{R_v} = 0 \Rightarrow \theta_v \left( C_v D + \frac{1}{R_v} + \frac{1}{R_m} \right) - \frac{\theta}{R_m} - \frac{\theta_b}{R_v} = 0 \Rightarrow$$

$$\Rightarrow C_v \frac{d\theta_v}{dt} + \left( \frac{1}{R_v} + \frac{1}{R_m} \right) \theta_v = \frac{\theta}{R_m} + \frac{\theta_b}{R_v}$$

**Ex.3**

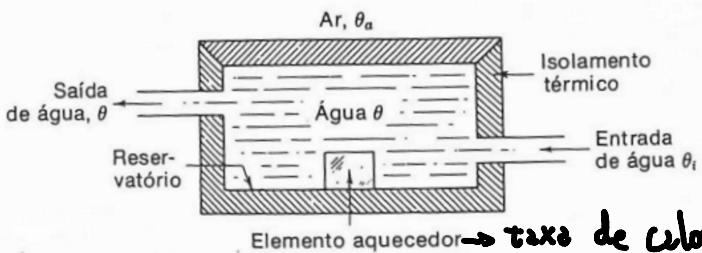


→ taxa de calor gerado:  $q$

• Pela 1ª Lei:


$$M \cdot C_p \cdot \dot{\theta} = q + m \cdot C_p \cdot (\theta_i - \theta) - \frac{\theta - \theta_i}{R} + i \overset{O \rightarrow \text{sem trabalho}}{\Rightarrow}$$

$$\Rightarrow M \cdot C_p \cdot \dot{\theta} + \left( m \cdot C_p + \frac{1}{R} \right) \theta = \left( m \cdot C_p + \frac{1}{R} \right) \theta_i + q$$

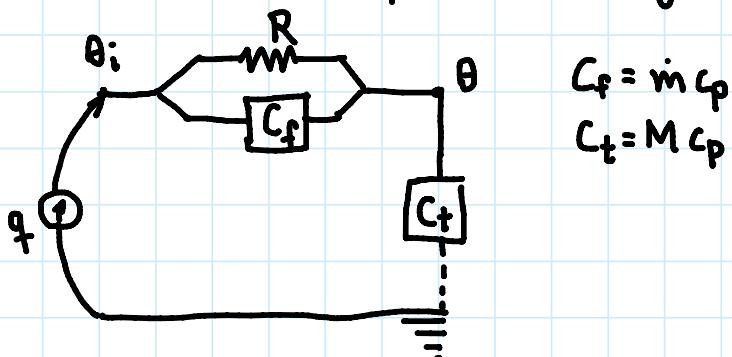
a) Circuito térmico equivalente (analogia tipo 2):



b) Circuito elétrico equivalente tipo 2:

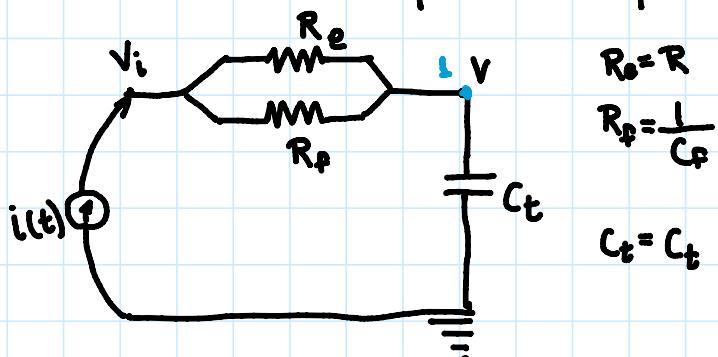

• Circuito elétrico equivalente tipo 1:

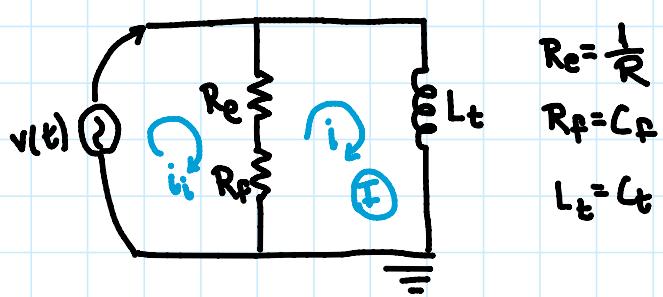

c) Pelo método prático:

→ Nô 1:

$$V \cdot \left( C_t D + \frac{1}{R_p} + \frac{1}{R_e} \right) - V_i \left( \frac{1}{R_p} + \frac{1}{R_e} \right) = i(t) \Rightarrow \theta \cdot \left( C_t D + C_p + \frac{1}{R} \right) - \theta_i \left( C_p + \frac{1}{R} \right) = q \Rightarrow$$

$$\Rightarrow C_t \cdot \dot{\theta} + \left( C_p + \frac{1}{R} \right) \theta = q + \left( C_p + \frac{1}{R} \right) \theta_i \Rightarrow M \cdot C_p \cdot \dot{\theta} + \left( m \cdot C_p + \frac{1}{R} \right) \theta = \left( m \cdot C_p + \frac{1}{R} \right) \theta_i + q$$

→ Masse(I):

$$i \cdot (L_t D + R_f + R_e) - i_i (R_f + R_e) = V(t) \Rightarrow \Theta \cdot (C_t D + C_f + \frac{1}{R}) - \Theta_i (C_f + \frac{1}{R}) = q \Rightarrow$$

$$\Rightarrow C_t \dot{\Theta} + (C_f + \frac{1}{R}) \Theta = q + (C_f + \frac{1}{R}) \Theta_i \Rightarrow \boxed{M c_p \cdot \dot{\Theta} + (m c_p + \frac{1}{R}) \Theta = (m c_p + \frac{1}{R}) \Theta_i + q}$$